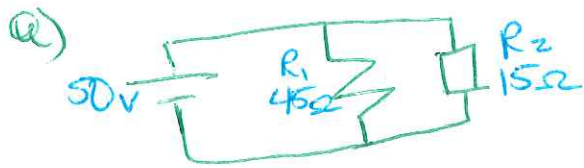




1. A  $45\ \Omega$  resistor and a  $15\ \Omega$  motor are connected in parallel with a switch to a  $50\text{V}$  battery



b)  $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$

$$\frac{1}{R_T} = \frac{1}{45} + \frac{1}{15}$$

$$\frac{1}{R_T} = .02 + .06$$

$$\frac{1}{R_T} = .08 \text{ flip}$$

$$R_T = \frac{1}{.08} = 11.25\ \Omega$$

c)  $I_T = I_1 + I_2 + \dots$

$$V = IR \quad I = \frac{V}{R}$$

$$I_1 = \frac{V_1}{R_1} = \frac{50}{45} = 1.1\text{A}$$

$$I_2 = \frac{V_2}{R_2} = \frac{50}{15} = 3.3\text{A}$$

$$I_T = 4.4\text{A}$$

d)  $V_T = V_1 = V_2$

$$V_T = I_T R_T$$

$$V_T = 4.44(11.25)$$

$$V_T = 49.9 = 50\text{V battery}$$

e)  $P = IV$

$$P_1 = I_1 V_1 = (1.1)(50) = 55.56\text{W}$$

$$P_2 = I_2 V_2 = (3.3)(50) = 166.7\text{W}$$

$$222.26\text{W}$$


f)  $P_T = I_T V_2$

$$P_T = 4.44(50) = 222.2\text{W}$$

[OR]

$$P_T = P_1 + P_2 + \dots$$

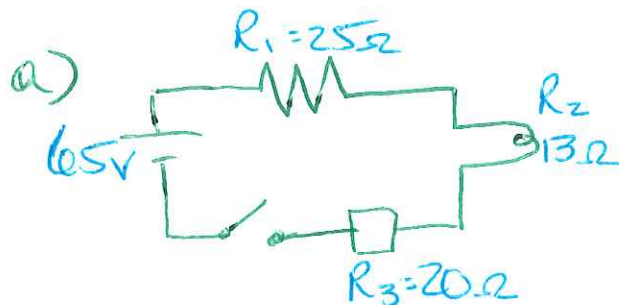2. A  $25\ \Omega$  resistor,  $13\ \Omega$  lamp, and a  $20\ \Omega$  motor are connected in parallel to a  $65\ \text{V}$  battery



b)  $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

$$\frac{1}{R_T} = \frac{1}{25} + \frac{1}{13} + \frac{1}{20}$$

$$\frac{1}{R_T} = .04 + .0769 + .05$$

$$\frac{1}{R_T} = \frac{0.1669}{1} \text{ flip}$$

$$\frac{R_T}{1} = \frac{1}{0.1669} = \boxed{5.992\ \Omega}$$

c)  $I_T = I_1 + I_2$

$$V_i = I_i R_i \quad I_i = \frac{V_i}{R_i}$$

$$I_1 = \frac{65}{25} = \boxed{2.6\ \text{A}}$$

$$I_2 = \frac{65}{13} = \boxed{5\ \text{A}}$$

$$I_3 = \frac{65}{20} = \boxed{3.25\ \text{A}}$$

$$\boxed{I_T = 10.85\ \text{A}}$$

d)  $V_T = V_1 = V_2 = \dots$

$$\boxed{V_T = 65\ \text{V}} = \text{battery}$$

e)  $P = IV \quad P_T = P_1 + P_2 + \dots$

$$P_1 = I_1 V_1 = 2.6(65) = \boxed{169\ \text{W}}$$


$$P_2 = I_2 V_2 = 5(65) = \boxed{325\ \text{W}}$$

$$P_3 = I_3 V_3 = 3.25(65) = \boxed{211.75\ \text{W}}$$

f)  $P_T = P_1 + P_2 + P_3 + \dots$

$$\boxed{P_T = 705.75\ \text{W}}$$

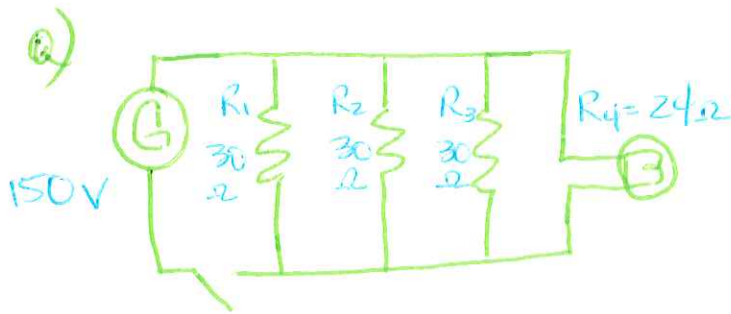3. Three  $R_1, R_2, R_3$   $30\ \Omega$  resistors and  $R_4$   $24\ \Omega$  lamp are connected in parallel with a switch to a 150V generator.



b)

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$

$$\frac{1}{R_T} = \frac{1}{30} + \frac{1}{30} + \frac{1}{30} + \frac{1}{24}$$

$$\frac{1}{R_T} = .0\bar{3} + .0\bar{3} + .0\bar{3} + .041\bar{6}$$

$$\frac{1}{R_T} = \frac{.141\bar{6}}{1} \text{ p.p.p}$$

$$R_T = \frac{1}{.141\bar{6}} = 7.058\ \Omega$$

c)  $I_T = I_1 + I_2 + I_3 \dots$

$$V = IR$$

$$I_1 = \frac{V_1}{R_1} = \frac{150}{30} = 5\text{A}$$

$$I_2 = \frac{V_2}{R_2} = \frac{150}{30} = 5\text{A}$$

$$I_3 = \frac{V_3}{R_3} = \frac{150}{30} = 5\text{A}$$

$$I_4 = \frac{V_4}{R_4} = \frac{150}{24} = 6.25\text{A}$$

d)  $V_T = V_1 = V_2 = \dots$

$$V_T = 150\text{V} = \text{battery}$$

e)  $P = IV$

$$P_1 = I_1 V_1 = 5(150) = 750\text{W}$$

$$P_2 = I_2 V_2 = 5(150) = 750\text{W}$$

$$P_3 = I_3 V_3 = 5(150) = 750\text{W}$$


$$P_4 = I_4 V_4 = 6.25(150) = 937.5$$

f)  $P_T = P_1 + P_2 + P_3 \dots$

$$P_T = 3187.5\text{W}$$



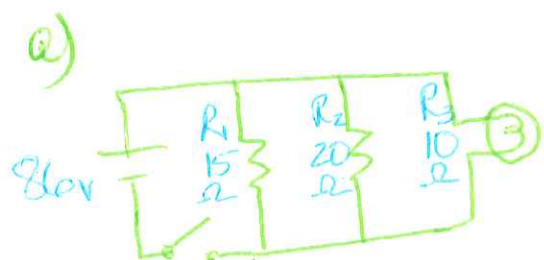4. A  $15\ \Omega$  resistor, a  $20\ \Omega$  resistor, and a  $10\ \Omega$  lamp are connected in parallel with a switch to a  $86\ \text{V}$  battery



b)  $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$

$\frac{1}{R_T} = \frac{1}{15} + \frac{1}{20} + \frac{1}{10}$

$\frac{1}{R_T} = .06 + .05 + .1 = .21$

$\frac{P}{R_T} = \frac{.21}{1} \text{ p/p}$       $\frac{R_T}{1} = \frac{1}{.21} = 4.77\ \Omega$

c)  $I_T = I_1 + I_2 + I_3 + \dots$

$V = IR$       $I = \frac{V}{R}$

$I_1 = \frac{V_1}{R_1} = \frac{86}{15} = 5.73\ \text{A}$

$I_2 = \frac{V_2}{R_2} = \frac{86}{20} = 4.3\ \text{A}$

$I_3 = \frac{V_3}{R_3} = \frac{86}{10} = 8.6\ \text{A}$

d)  $V_T = V_1 = V_2$

$V_T = 86\ \text{V} = \text{battery}$

e)  $P = IV$

$P_1 = I_1 V_1 = 5.73(86) = 492.78\ \text{W}$

$P_2 = I_2 V_2 = 4.3(86) = 369.8\ \text{W}$

$P_3 = I_3 V_3 = 8.6(86) = 739.6\ \text{W}$

$P_T = 1602.18\ \text{W}$

f)  $P_T = P_1 + P_2 + P_3$