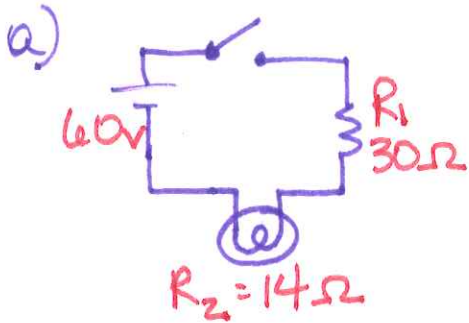


Circuit Practice

1. 30Ω resistor + a 14Ω lamp are connected in series with a switch + 60V battery



b) $R_T = R_1 + R_2 + \dots$
 $R_T = 30 + 14 = 44\Omega$

c) $I_T = I_1 = I_2 = \dots$

$$V_T = I_T R_T$$

$$60 = I_T 44$$

$$I_T = \frac{60}{44} = 1.36A$$

d) $V_T = V_1 + V_2 + \dots$

$$V_1 = I_1 R_1$$

$$V_1 = 1.36(30) = 40.8V$$

$$V_2 = I_2 R_2$$

$$V_2 = 1.36(14) = 19.04V$$

e) $P = IV$

$$P_1 = I_1 V_1$$

$$P_1 = 1.36(40.8) = 55.48W$$

$$P_2 = I_2 V_2$$

$$P_2 = 1.36(19.04) = 25.89W$$


f) $P_T = I_T V_T$

OR

$$P_T = P_1 + P_2 + \dots$$

$$P_T = 55.48 + 25.89 = 81.37W$$

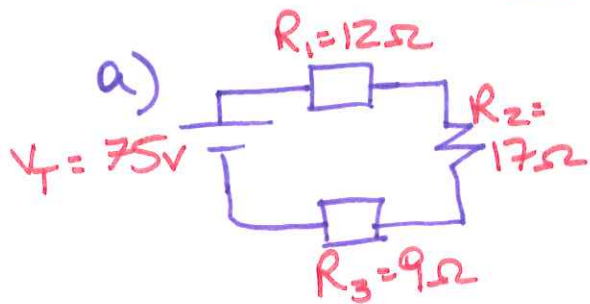2. 12Ω motor + a 17Ω resistor + a 9Ω motor are connected in series to a $75V$ battery



b) $R_T = R_1 + R_2 + \dots$
 $R_T = 12 + 17 + 9 =$
 $R_T = 38\Omega$

c) current is the same everywhere in series
 $I_T = I_1 = I_2 = \dots$

$V_T = I_T \cdot R_T$ ← dont use R_1 be consistent $I_T = I_1$
 $I_1 = I_T = \frac{V_T}{R_T} = \frac{75}{38} = \underline{1.97A}$
 ↑ dont use R_1

d) $V_T = V_1 + V_2 + \dots$

$V_1 = I_1 R_1$
 $V_1 = (1.97)(12) = \underline{23.64V}$
 $V_2 = (1.97)(17) = \underline{33.49V}$
 $V_3 = (1.97)(9) = \underline{17.73V}$

e) $P = IV$

$P_1 = I_1 V_1 = (1.97)(23.64) = \underline{46.57W}$

$P_2 = I_2 V_2 = (1.97)(33.49) = \underline{65.98W}$

$P_3 = I_3 V_3 = (1.97)(17.73) = \underline{34.93W}$

$P_T = \underline{147.48W}$

f) $P_T = I_T V_T$
OR


$P_T = P_1 + P_2 + \dots$

c) $I_T = I_1 = I_2 = I_3$

$V_1 = I_1 R_1$

$I_1 = \frac{V_1}{R_1}$

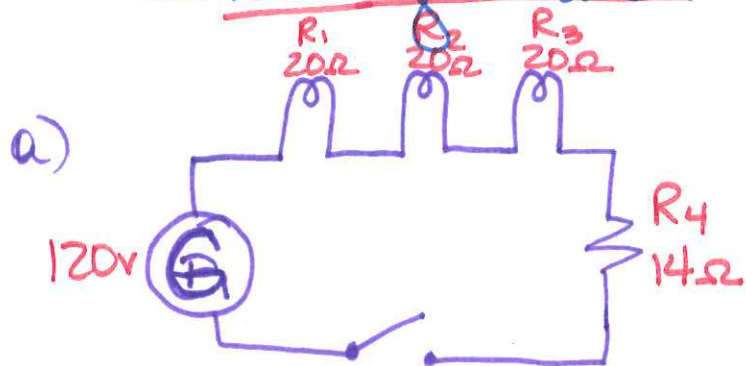3. Three 20Ω lamps and a 14Ω resistor are connected in series with a switch to a 120V generator



b)

$$R_T = R_1 + R_2 + \dots$$

$$R_T = 20 + 20 + 20 + 14$$

$$R_T = 74\Omega$$

c)

$$I_T = I_1 = I_2$$

$$V = IR$$

$$I_T = \frac{V_T}{R_T} = \frac{120}{74} = 1.62\text{A}$$

d)

$$V_T = V_1 + V_2 + \dots$$

$$V_1 = I_1 R_1$$

$$V_1 = (1.62)20 = 32.4\text{V}$$

$$V_2 = (1.62)20 = 32.4\text{V}$$

$$V_3 = (1.62)20 = 32.4\text{V}$$

$$V_4 = (1.62)14 = 22.68\text{V}$$

e)

$$P = IV$$

$$P_1 = I_1 V_1 = (1.62)(32.4) = 52.488\text{W}$$

$$P_2 = I_2 V_2 = (1.62)(32.4) = 52.488\text{W}$$

$$P_3 = I_3 V_3 = (1.62)(32.4) = 52.488\text{W}$$

$$P_4 = I_4 V_4 = (1.62)(22.68) = 36.7416\text{W}$$

$$P_T = 194.21\text{W}$$


f)

$$P_T = I_T V_T$$

OR

$$P_T = P_1 + P_2$$

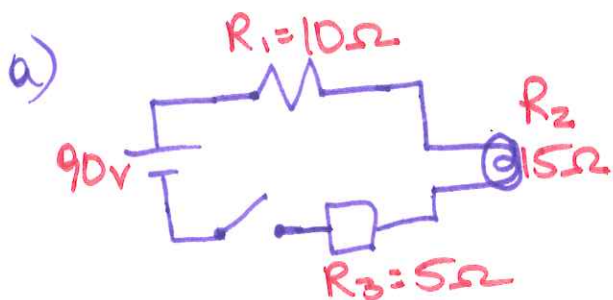4) A $10\text{-}\Omega$ resistor, $15\text{-}\Omega$ lamp, $5\text{-}\Omega$ motor are connected in series with a switch and a 90V battery.



b) $R_T = R_1 + R_2 + \dots$
 $R_T = 10 + 15 + 5 = 30\Omega$

c) $I_T = I_1 = I_2$
 $V = IR$
 $I_2 = I_T = \frac{V_T}{R_T} = \frac{90}{30} = 3\text{A}$

d) $V_T = V_1 + V_2 + \dots$
 $V = IR$
 $V_1 = I_1 R_1 = 3(10) = 30\text{V}$
 $V_2 = I_2 R_2 = 3(15) = 45\text{V}$
 $V_3 = I_3 R_3 = 3(5) = 15\text{V}$

e) $P = IV$
 $P_1 = I_1 V_1 = 3(30) = 90\text{W}$
 $P_2 = I_2 V_2 = 3(45) = 135\text{W}$
 $P_3 = I_3 V_3 = 3(15) = 45\text{W}$

f) $P_T = I_T V_T$
 $P_T = 3(90) = 270$
 10R

$P_T = P_1 + P_2 + \dots$
 $P_T = 270\text{W}$